


# Lecture 21, Mar 7, 2022
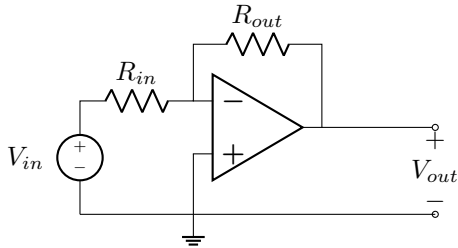
## Operational Amplifiers (Op-Amps)

- Op amps have 3 terminals that are relevant for this course: the positive (non-inverting) terminal, the negative (inverting) terminal, and then output terminal
  - Inverting input has voltage  $v_1$  and current  $i_2$ , non-inverting input has voltage  $v_2$  and current  $i_1$ ; output has voltage  $v_{out}$  and current  $i_{out}$  (voltages measured wrt ground)
  - The symbol is




- If there is a path between the inverting input and output (either a short or any resistance), then the op amp as a *negative feedback connection*
  - Under a negative feedback connection,  $v_1 = v_2$ , i.e. it forces 2 voltages to be the same (under ideal conditions), and  $i_1 = i_2 = 0$  (infinite input impedance)
- In this course we only discuss ideal op amps
- Example circuit:



- The path from the output to the inverting input forces  $v_2 = v_1$ , therefore the current through  $R_{in}$  is  $\frac{V_{in}}{R_{in}}$ 
  - No current goes into the op amp so current through  $R_f$  is also  $I_{in}$
  - Since  $v_2 = 0$  the current through  $R_f$  is also  $-\frac{V_{out}}{R_f}$
  - Equating these currents:  $\frac{V_{in}}{R_{in}} = I_{in} = \frac{V_{out}}{R_f} \implies \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}$
  - This circuit is called an *inverting amplifier* since it switches the polarity, and amplifies it by a gain of  $-\frac{R_f}{R_{in}}$

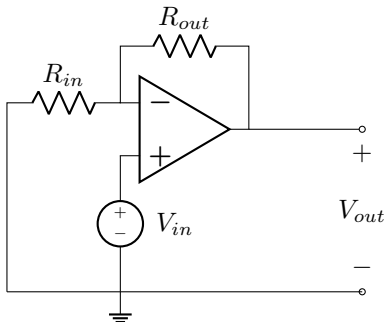- If the input voltage now goes into the noninverting input, the output voltage is no longer inverted, so this is now a *noninverting amplifier*:



- In general, to solve an op amp circuit when there is a connection from output to inverting input, first try to find either  $v_1$  or  $v_2$ , and then use the relationship  $v_1 = v_2$  to find the voltage at the other terminal, and then solve the rest of the circuit